



UNIT 12

Registers and Counters

This chapter includes:

12.1 Registers and Register Transfers

12.2 Shift Registers

12.3 Design of Binary Counters

12.4 Counters for Other Sequences

12.5 Counter Design using S-R and J-K Flip-Flops

12.6 Derivation of Flip-Flop Input Equations-Summary

Learning Objectives

1. Explain the operation of registers. Show how to transfer data between registers using a tri-state bus.
2. Explain the operation of shift registers, show how to build them using flip-flops, and analyze their operation. Construct a timing diagram for a shift register.
3. Explain the operation of binary counters, show how to build them using flip-flops and gates, and analyze their operation.

Learning Objectives

4. Given the present state and desired next state of a flip-flop, determine the required flip-flop inputs.
5. Given the desired counting sequence for a counter, derive the flip-flop input equations.
6. Explain the procedures used for deriving flip-flop input equations.
7. Construct a timing diagram for a counter by tracing signals through the circuit.

Registers and Register Transfers

Introduction:


- ❖ A **register** consists of a group of flip-flops with a common clock input. Registers are commonly used to store and shift binary data.
- ❖ A **counter** is usually constructed from two or more flip-flops which change states in a prescribed sequence when input pulses are received.

Registers and Register Transfers

4-Bit D Flip-Flop Registers with Data, Load, Clear and Clock Inputs:


FIGURE 12-1
4-Bit D Flip-Flop
Registers with Data,
Load, Clear, and
Clock Inputs

© Cengage Learning 2014

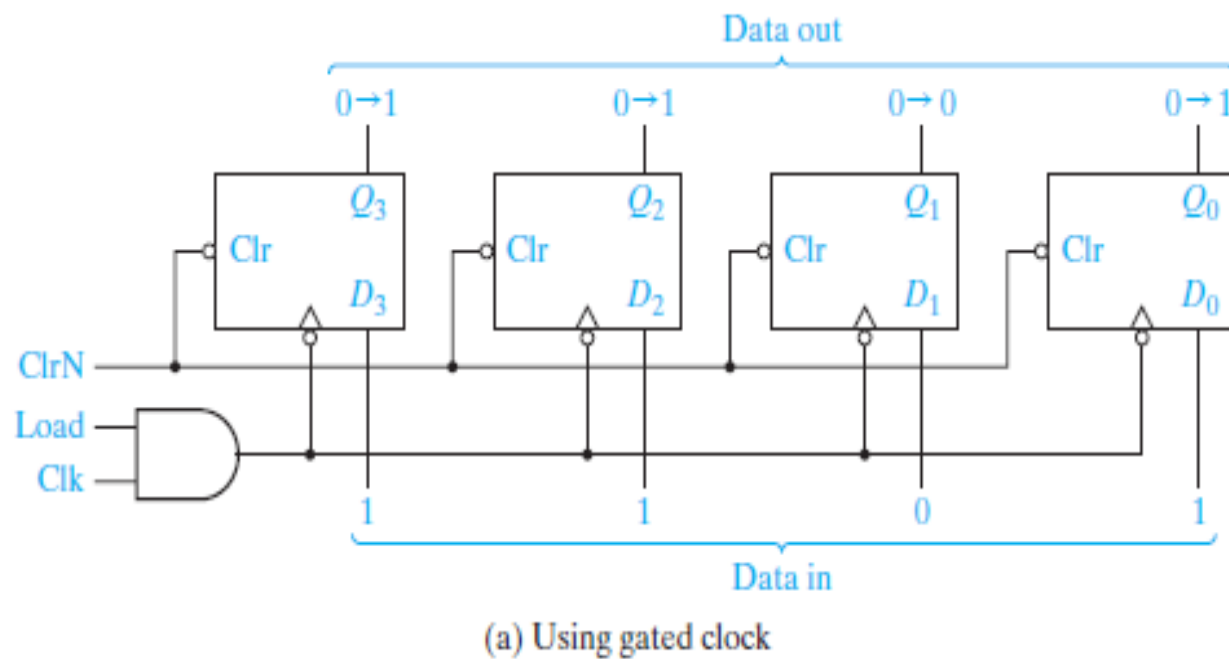


Registers and Register Transfers

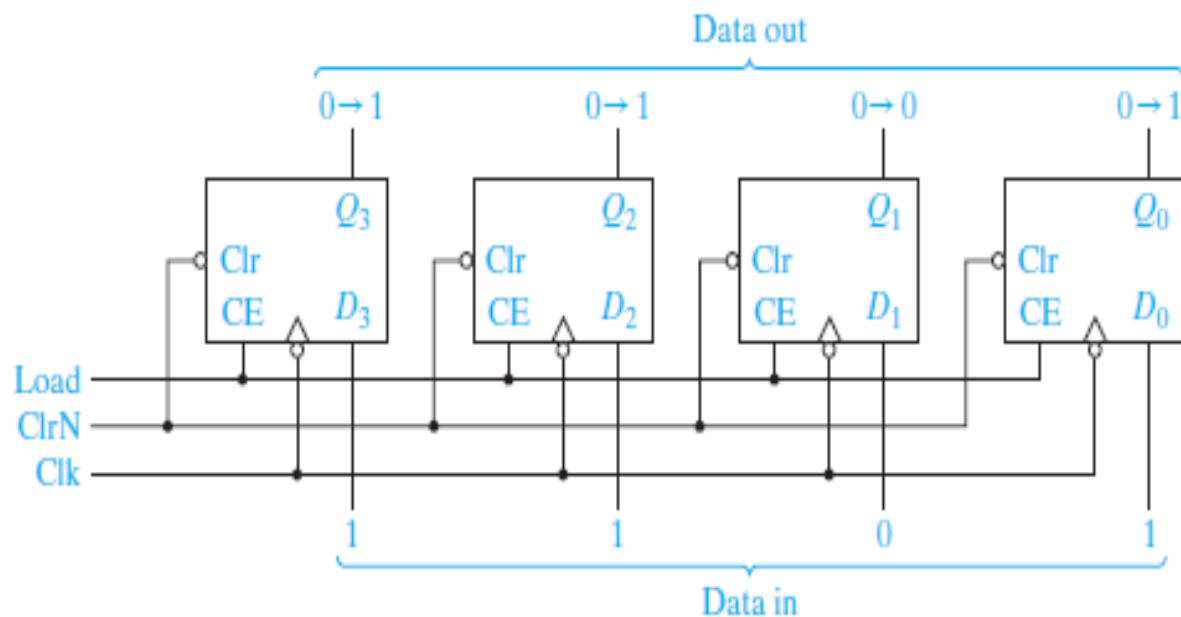4-Bit D Flip-Flop Registers with Data, Load, Clear and Clock Inputs (continued):



(b) With clock enable

 


(c) Symbol

Registers and Register Transfers

Data Transfer Between Registers:

FIGURE 12-2
Data Transfer
Between Registers

© Cengage Learning 2014

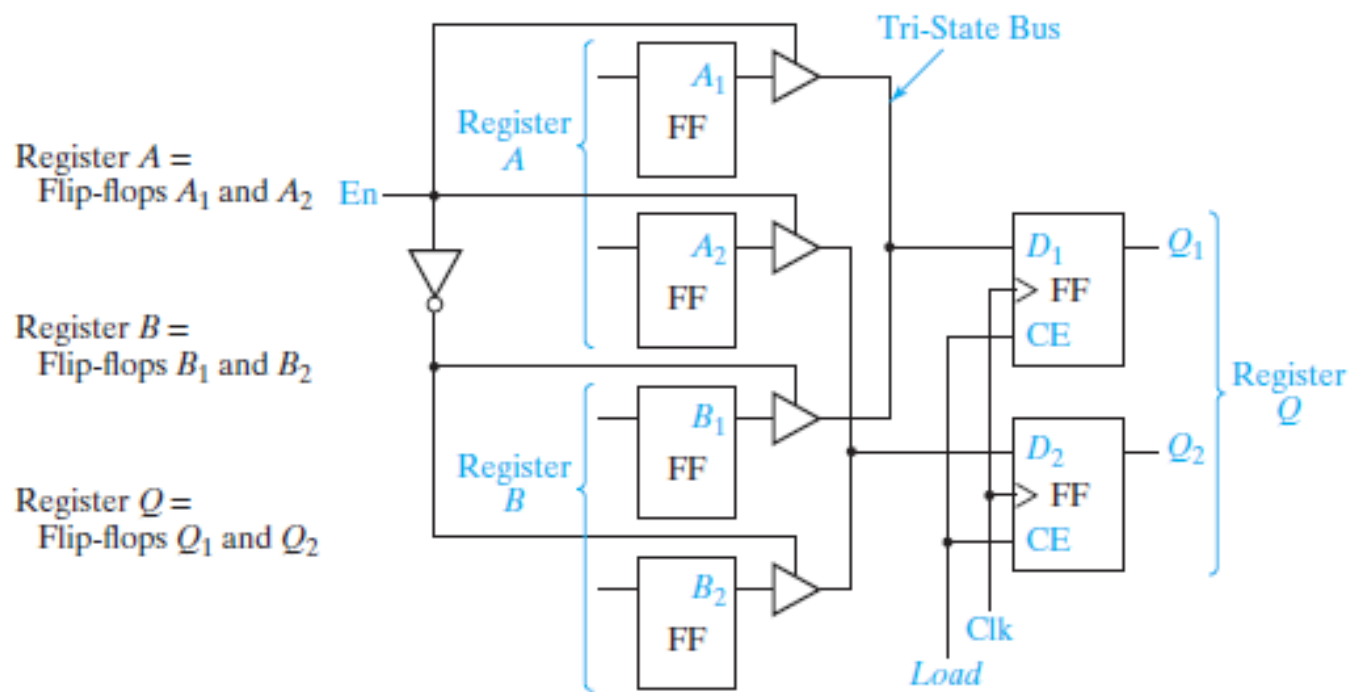


Registers and Register Transfers

8-Bit Register with Tri-State Output:

❖ Figure 12-3(a) shows an integrated circuit register that contains eight D flip-flops with tri-state buffers at the flip-flop outputs.

❖ These buffers are enabled when $En = 0$. A symbol for this 8-bit register is shown in Figure 12-3(b).

FIGURE 12-3
Logic Diagram for
8-Bit Register with
Tri-State Output
© Cengage Learning 2014

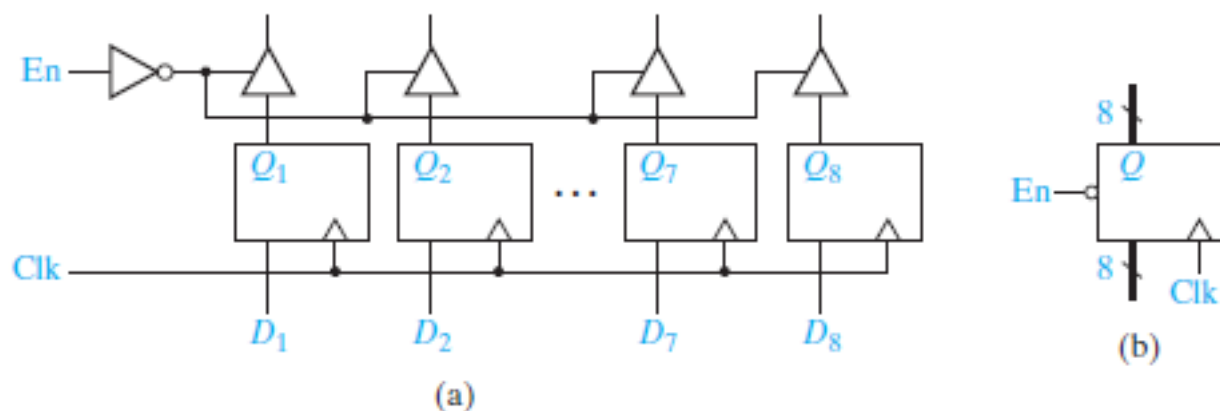


Registers and Register Transfers

Data Transfer Using a Tri-State Bus:

FIGURE 12-4
Data Transfer Using
a Tri-State Bus

© Cengage Learning 2014

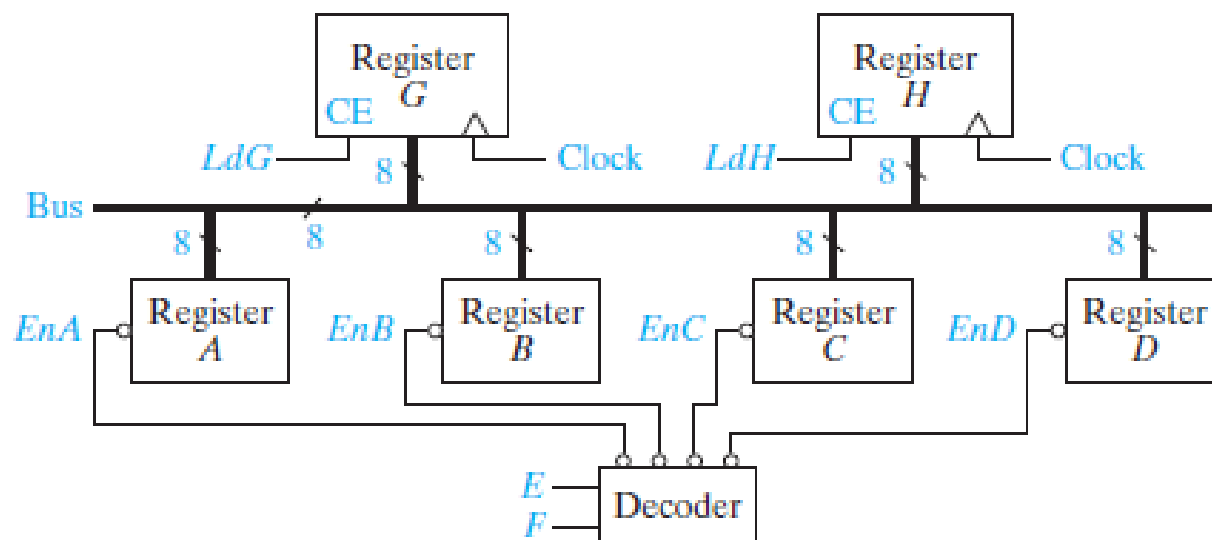

Operation is as follows:

- If $EF = 00$, A is stored in G (or H).
- If $EF = 01$, B is stored in G (or H).
- If $EF = 10$, C is stored in G (or H).
- If $EF = 11$, D is stored in G (or H).


Registers and Register Transfers

Parallel Adder with Accumulator:

❖ It is frequently desirable to store one number in a register of flip-flops (called an **accumulator**) and add a second number to it, leaving the result stored in the accumulator. See figure 12-5 below:

FIGURE 12-5 *n*-Bit Parallel Adder with Accumulator

© Cengage Learning 2014

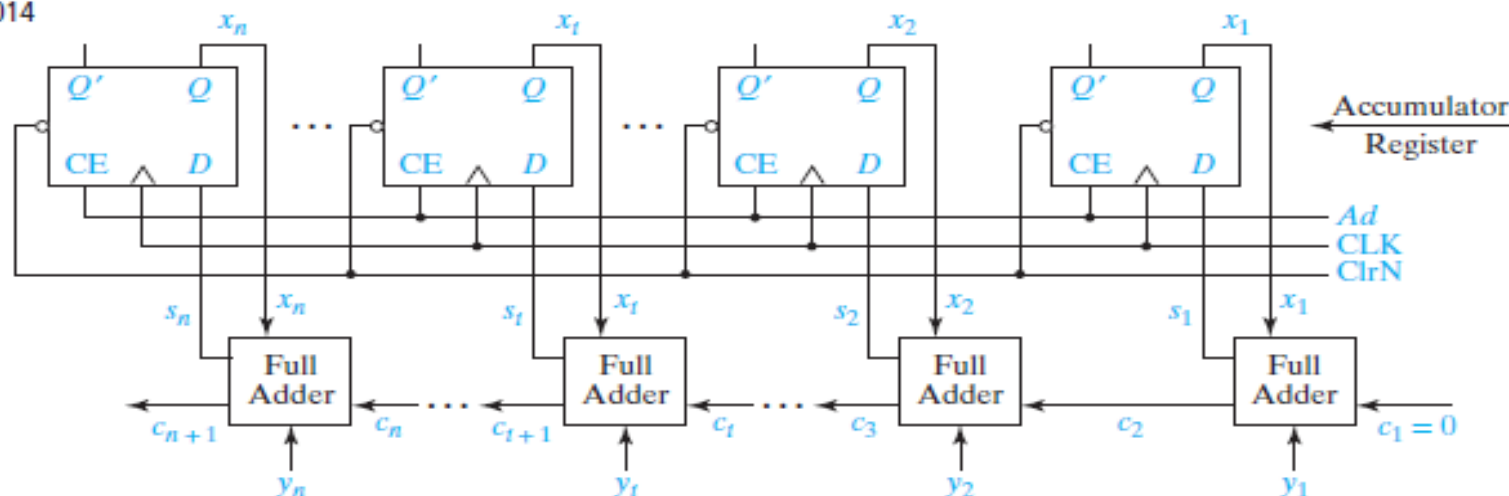


Registers and Register Transfers

Adder Cell with Multiplexer:

❖ Figure 12-6 shows a typical cell of the adder where the accumulator flip-flop can either be loaded directly from y_i or from the sum output (s_i).

FIGURE 12-6
Adder Cell with
Multiplexer
© Cengage Learning 2014

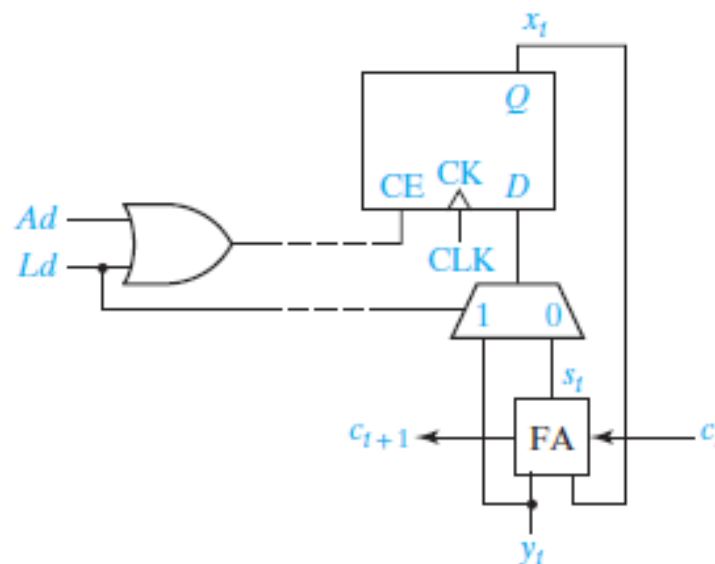

Shift Registers


Shift Registers:

- ❖ A shift register is a register in which binary data can be stored, and this data can be shifted to the left or right when a shift signal is applied.
- ❖ Shifts can be linear or cyclic.
- ❖ The figure on the next slide shows a 4-bit right-shift register with serial input and output constructed from D flip-flops.
- ❖ When Shift=1, the clock is enabled and shifting occurs on the rising clock edge. When Shift=0, no shifting occurs and the data in the register is unchanged.


Shift Registers

FIGURE 12-7
Right-Shift
Register

© Cengage Learning 2014

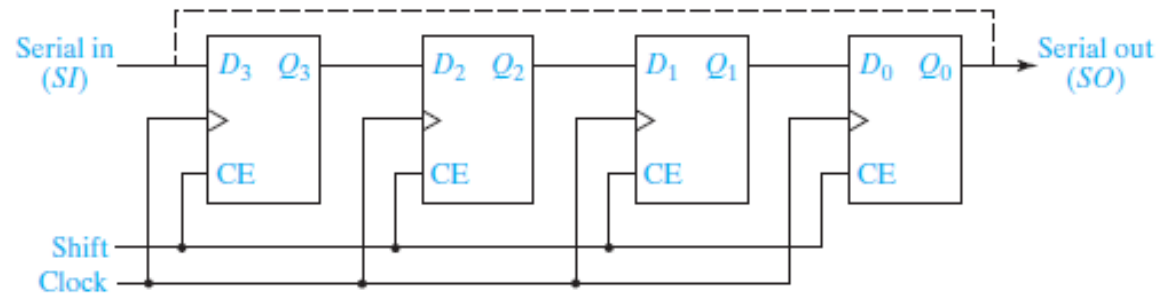

(a) Flip-flop connections

 

(b) Timing diagram

Shift Registers

Serial In/ Serial Out Registers:

❖ **Serial in** means that data is shifted into the first flip-flop one bit at a time, and the flip-flops cannot be loaded in parallel.

❖ **Serial out** means that data can only be read out of the last flip-flop and the outputs from the other flip-flops are not connected to terminals of the integrated circuit.

Shift Registers

FIGURE 12-8
8-Bit Serial-In,
Serial-Out Shift
Register

© Cengage Learning 2014


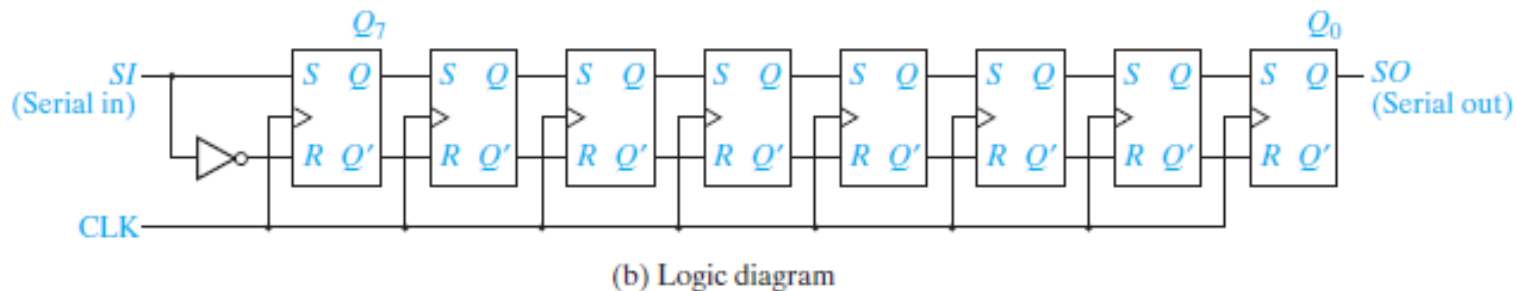
 


FIGURE 12-9
Typical Timing
Diagram for
Shift Register of
Figure 12-8

© Cengage Learning 2014

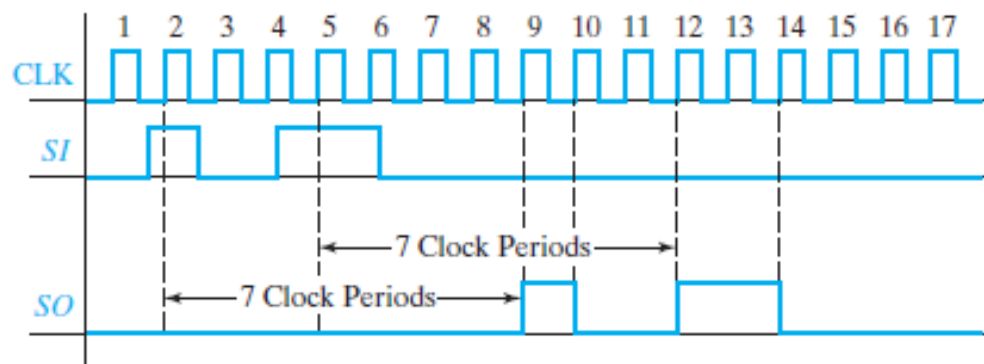


Shift Registers


FIGURE 12-10

Parallel-In,
Parallel-Out
Right-Shift
Register

© Cengage Learning 2014

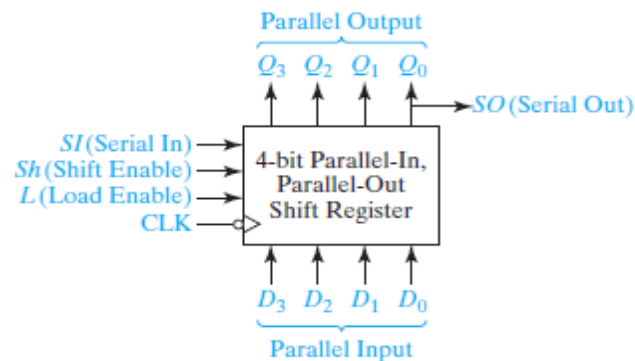

(a) Block diagram

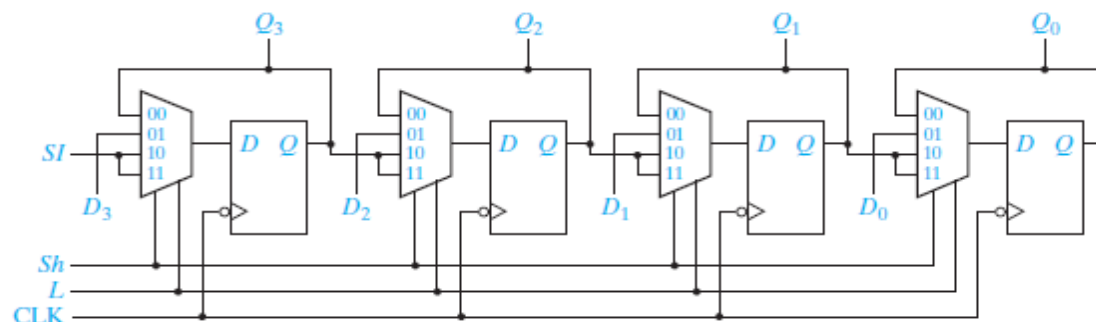

(b) Implementation using flip-flops and MUXes

The next-state equations for the flip-flops are

$$Q_3^+ = Sh' \cdot L' \cdot Q_3 + Sh' \cdot L \cdot D_3 + Sh \cdot SI \quad (12-1)$$

$$Q_2^+ = Sh' \cdot L' \cdot Q_2 + Sh' \cdot L \cdot D_2 + Sh \cdot Q_3$$

$$Q_1^+ = Sh' \cdot L' \cdot Q_1 + Sh' \cdot L \cdot D_1 + Sh \cdot Q_2$$

$$Q_0^+ = Sh' \cdot L' \cdot Q_0 + Sh' \cdot L \cdot D_0 + Sh \cdot Q_1$$

Shift Registers

TABLE 12-1


Shift Register

© Cengage Learning

FIGURE 12-11

Timing Diagram for Shift Register

© Cengage Learning 2014

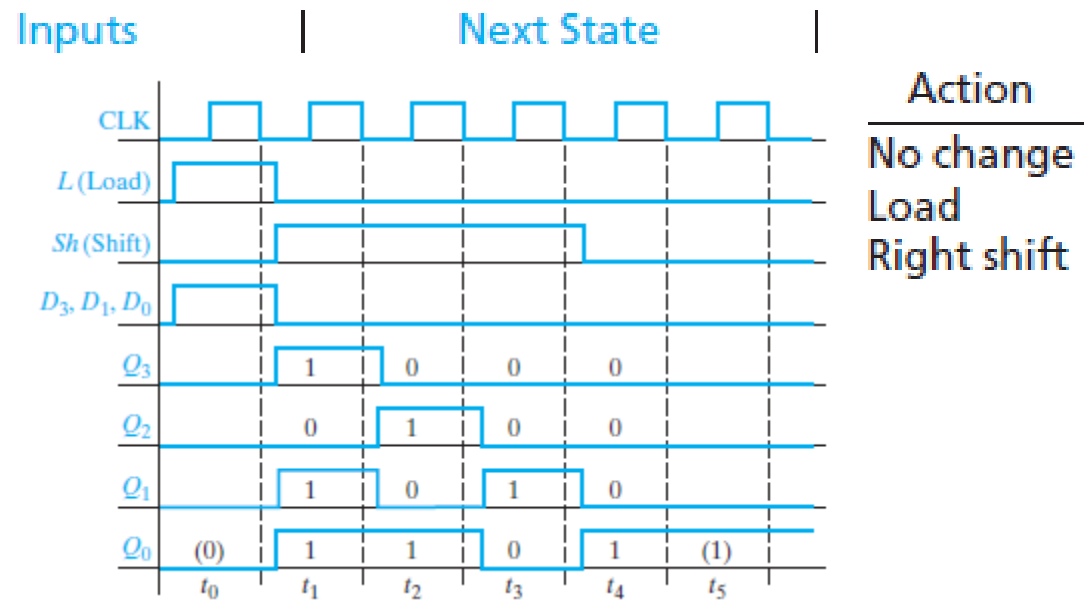


Shift Registers

Johnson Counter:


- ❖ A circuit that cycles through a fixed sequence of states is called a **counter**.
- ❖ A shift register with inverted feedback is called a **Johnson counter** or a **twisted ring counter**.

FIGURE 12-12
Shift Register
with Inverted
Feedback

© Cengage Learning 2014

 

(a) Flip-flop connections

 


(b) Transition graph

Shift Registers

General Form of a Shift Register Counter:

FIGURE 12-13
General Shift
Register Counter

© Cengage Learning 2014

 

Design of Binary Counters

Synchronous and Ripple Counters:

- ❖ For synchronous counters, the operation of the flip-flops is synchronized by a common clock pulse so that when several flip-flops must change state, the state changes occur simultaneously.
- ❖ Ripple counters are those in which the state change of one flip-flop triggers another flip-flop. These will not be focused on in this chapter.

Design of Binary Counters


Binary Counters Using 3 T Flip-Flops to Count Clock Pulses:

- ❖ We assume that all the flip-flops change state a short time following the rising edge of the input pulse.
- ❖ The state of the counter is determined by the states of the individual flip-flops; for example, if flip-flop C is in state 0, B in state 1, and A in state 1, the state of the counter is 011.
- ❖ Initially, assume that all flip-flops are set to the 0 state. When a clock pulse is received, the counter will change to state 001; when a second pulse is received, the state will change to 010, etc.
- ❖ When 111 is reached, the counter resets to the 000 state.
- ❖ See next slide for figure.

Design of Binary Counters

FIGURE 12-14
Synchronous
Binary Counter

© Cengage Learning 2014

 

Design of Binary Counters

Design of Binary Counter Using Transition Tables:

- ❖ This table shows the present state of flip-flops C, B, and A (before a clock pulse is received) and the corresponding next state (after the clock pulse is received).
- ❖ A third column in the table is used to derive the inputs for T_C , T_B , and T_A . Whenever the entries in the A and A^+ columns differ, flip-flop A must change state and T_A must be 1.
- ❖ T_C , T_B , and T_A are now derived from the table as functions of C, B, and A.

TABLE12-2
Transition Table for
Binary Counter
© Cengage Learning 2014


Present State			Next State			Flip-Flop Inputs		
C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Design of Binary Counters

Karnaugh Maps for Binary Counters:

❖ Figure 12-15 shows the Karnaugh maps for T_C and T_B , from which $T_C = BA$ and $T_B = A$. These equations yield the same circuit derived previously for Figure 12-14.

FIGURE 12-15
Karnaugh Maps
for Binary Counter
© Cengage Learning 2014

 


Design of Binary Counters

Binary Counter with D Flip-Flops:

❖ We must convert each D flip-flop to a T flip-flop by adding an XOR (exclusive-OR) gate, as shown in Figure 11-28(b). Figure 12-16 shows the resulting counter circuit.

FIGURE 12-16
Binary Counter
with D Flip-Flops
© Cengage Learning 2014

 

Design of Binary Counters

We can also derive the D flip-flop inputs for the binary counter starting with its transition table (Table 12-2). For a D flip-flop, $Q^+ = D$. By inspection of the table, $Q_A^+ = A'$, so $D_A = A'$. The maps for Q_B^+ and Q_C^+ are plotted in Figure 12-17. The D input equations derived from the maps are


$$D_A = A^+ = A'$$

$$D_B = B^+ = BA' + B'A = B \oplus A \quad (12-2)$$

$$D_C = C^+ = C'BA + CB' + CA' = C'BA + C(BA)' = C \oplus BA$$

which give the same logic circuit as was obtained by inspection.

FIGURE 12-17
Karnaugh Maps
for D Flip-Flops
© Cengage Learning 2014

 


Design of Binary Counters

Binary Up-Down Counter:

FIGURE 12-19
Binary Up-Down
Counter


© Cengage Learning 2014

 

Design of Binary Counters

Up-Down Counter Transition Graph, Table and Logic Equations::

FIGURE 12-18
Transition Graph
and Table for
Up-Down
Counter
© Cengage Learning 2014

 

CBA	$C^+B^+A^+$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

The up-down counter can be implemented using D flip-flops and gates, as shown in Figure 12-19. The corresponding logic equations are

$$D_A = A^+ = A \oplus (U + D)$$

$$D_B = B^+ = B \oplus (UA + DA')$$


$$D_C = C^+ = C \oplus (UBA + DB'A')$$

Design of Binary Counters

Loadable Counter with Count Enable:

FIGURE 12-20
Loadable Counter
with Count Enable

© Cengage Learning 2014

 

(a)

ClrN	Ld	Ct	C ⁺	B ⁺	A ⁺	
0	X	X	0	0	0	
1	1	X	D _C	D _B	D _A	(load)
1	0	0	C	B	A	(no change)
1	0	1	Present state + 1			

(b)

The next-state equations for the counter of Figure 12-21 are

$$\begin{aligned}
 A^+ &= D_A = (Ld' \cdot A + Ld \cdot D_{Ain}) \oplus Ld' \cdot Ct \\
 B^+ &= D_B = (Ld' \cdot B + Ld \cdot D_{Bin}) \oplus Ld' \cdot Ct \cdot A \\
 C^+ &= D_C = (Ld' \cdot C + Ld \cdot D_{Cin}) \oplus Ld' \cdot Ct \cdot B \cdot A
 \end{aligned}$$


When $Ld = 0$ and $Ct = 1$, these equations reduce to $A^+ = A'$, $B^+ = B \oplus A$, and $C^+ = C \oplus BA$, which are the equations previously derived for a 3-bit counter.

Design of Binary Counters

FIGURE 12-21

Circuit for
Figure 12-20

© Cengage Learning 2014

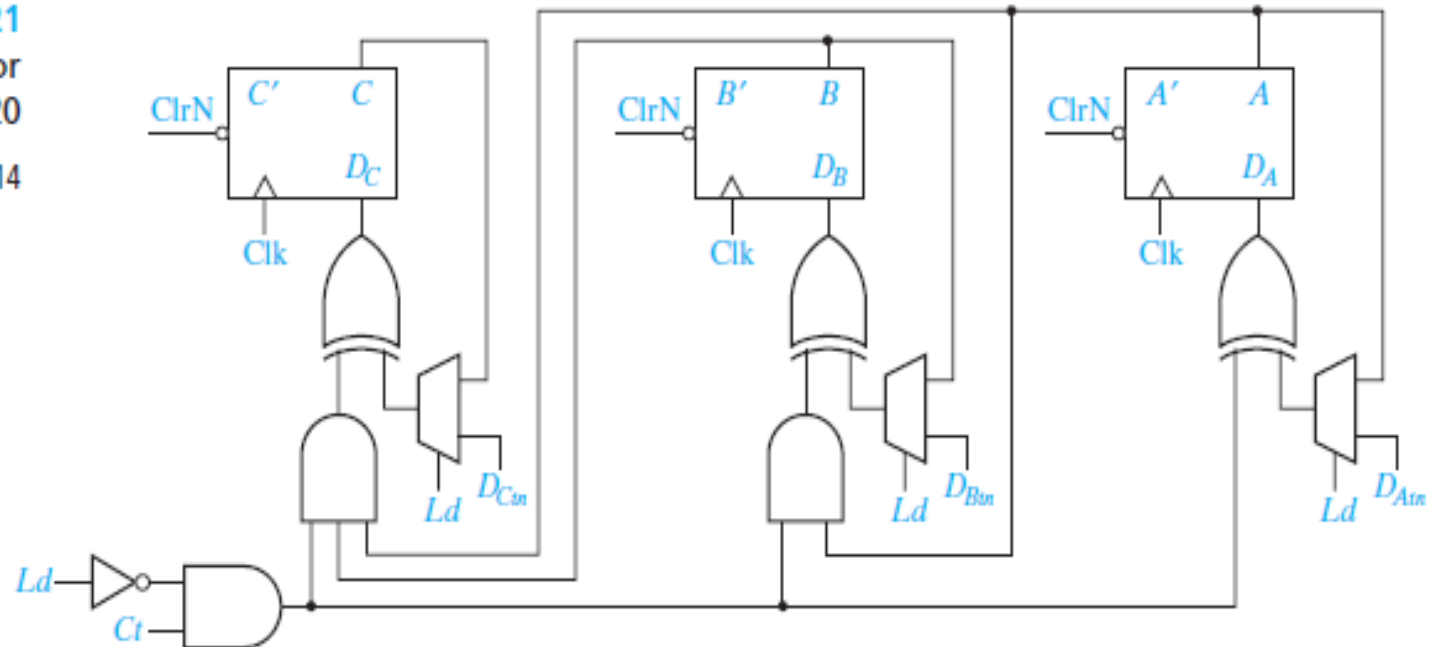


Counters for Other Sequences

Counter for Other Sequences (Example):

- ❖ We will design a counter for the transition table shown in Table 12-3 using T Flip-Flops.

FIGURE 12-22
Transition Graph
for Counter

 

© Cengage Learning 2014

TABLE 12-3
Transition Table for
Figure 12-22


© Cengage Learning 2014

C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	1	0	0
0	0	1	–	–	–
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	–	–	–
1	1	0	–	–	–
1	1	1	0	1	0


Counters for Other Sequences

FIGURE 12-23

© Cengage Learning 2014

 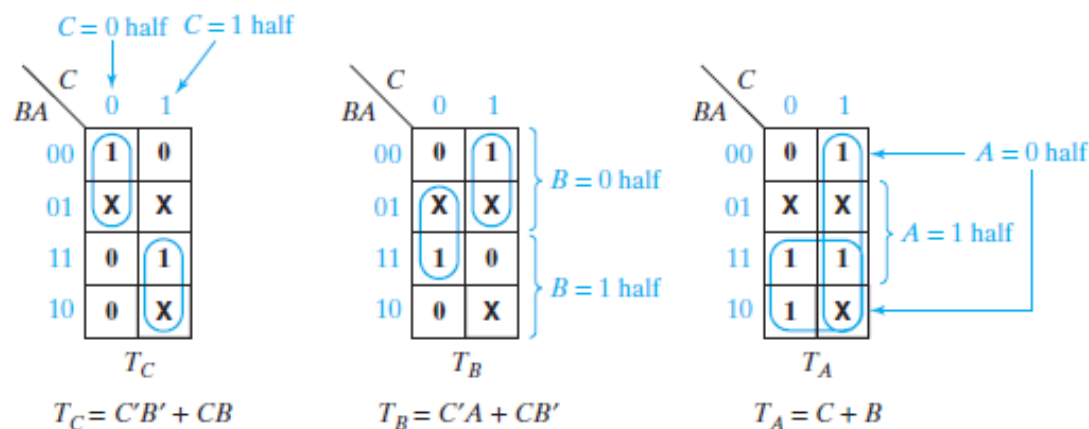

(a) Next-state maps for Table 12-3

(b) Derivation of T inputs

Counters for Other Sequences

Input for T Flip-Flop:

- ❖ $T=1$ whenever a state of change is required.

TABLE 12-4

Input for
T Flip-Flop

© Cengage Learning 2014


Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

$$T = Q^+ \oplus Q$$

Counters for Other Sequences

FIGURE 12-24
Counter Using
T Flip-Flops

© Cengage Learning 2014

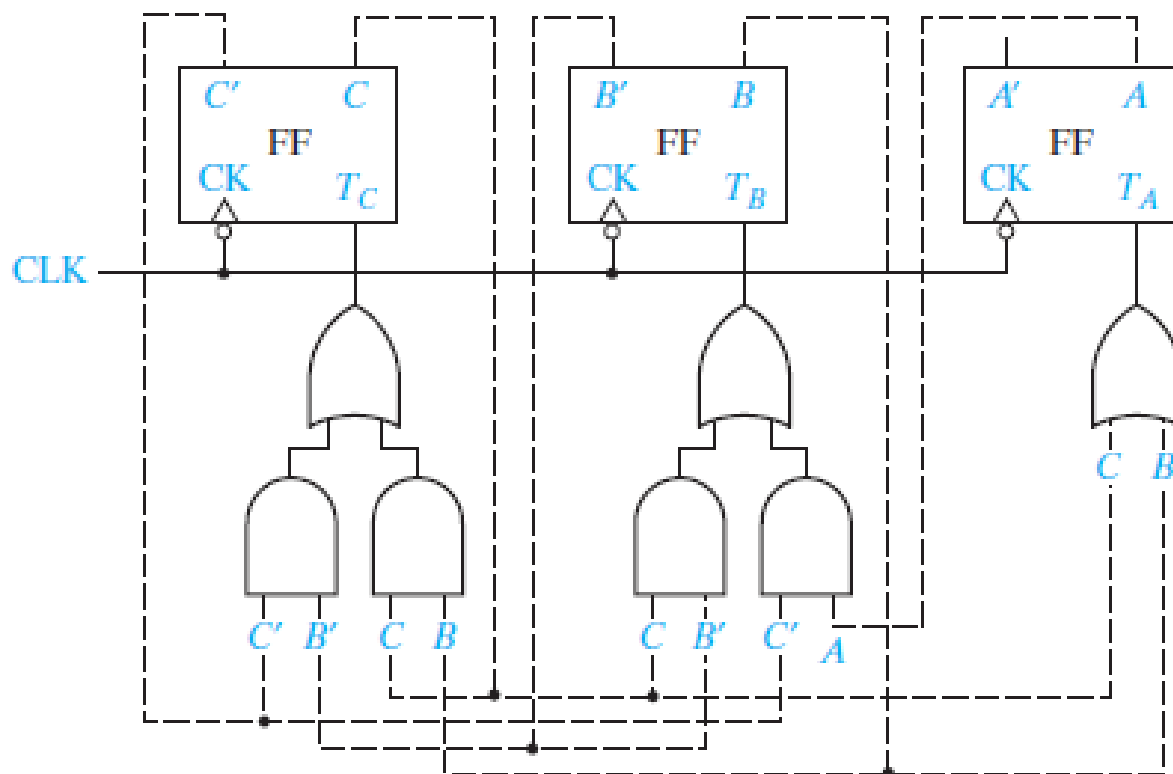


Counters for Other Sequences

FIGURE 12-25

Timing Diagram
for Figure 12-24

© Cengage Learning 2014

 

Counters for Other Sequences

Procedure for Designing a Counter Using T Flip-Flops:


1. Form a transition table which gives the next flip-flop states for each combination of present flip-flop states.
2. Plot the next-state maps from the table.
3. Plot a T input map for each flip-flop. When filling in the T_Q map, T_Q must be 1 whenever $Q^+ \neq Q$. This means that the T_Q map can be formed from the Q^+ map by complementing the $Q = 1$ half of the map and leaving the $Q = 0$ half unchanged.
4. Find the T input equations from the maps and realize the circuit.

Counters for Other Sequences

Counter Design using D Flip-Flops:

FIGURE 12-27
Counter of
Figure 12-22
Using D Flip-Flops

© Cengage Learning 2014

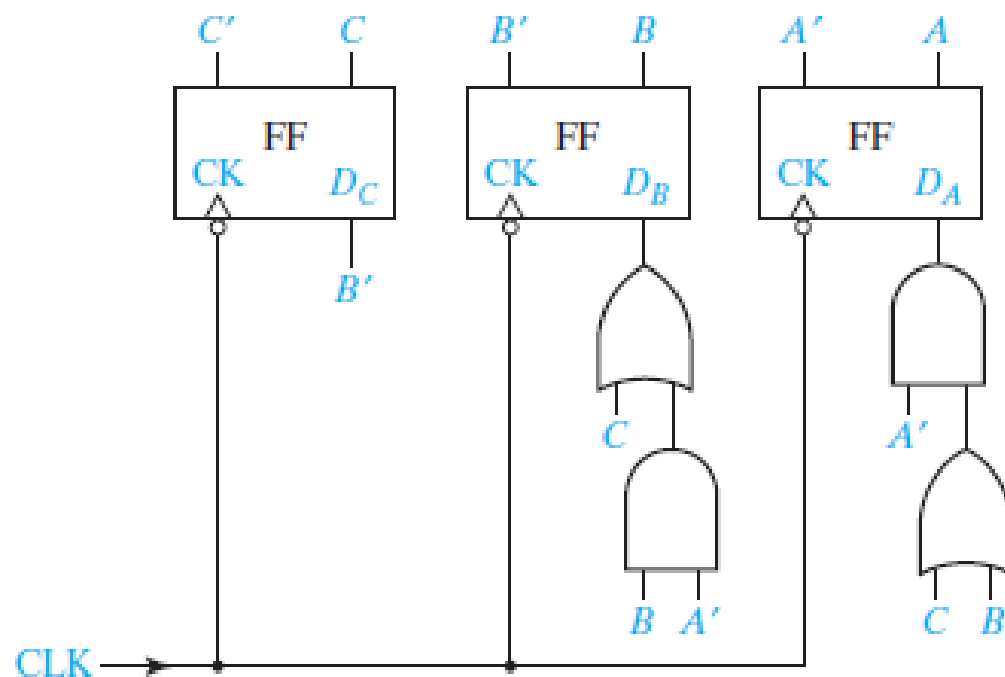


Counters for Other Sequences

Binary Counter with Clear:

- ❖ Counters and shift registers with clear, preset, or parallel load capability can also be used to generate nonbinary count cycles.
- ❖ Consider a binary counter with a clear input as shown Figure 12-28.

FIGURE 12-28
Binary Counter
with Clear

© Cengage Learning 2014

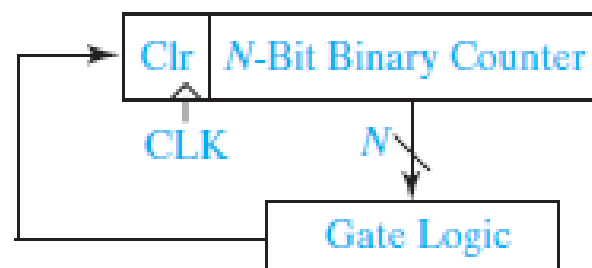

Synchronous Clear:

$$\text{Clr} = Q_3 Q_0$$


Asynchronous Clear:

$$\text{Clr} = Q_3 Q_1$$

Counters for Other Sequences

Binary Counter with Parallel Load:

FIGURE 12-29
Binary Counter
with Parallel Load
© Cengage Learning 2014

 

The counter must cycle through states 3 to 12. The logic must generate Ld when the counter is in state 12 and the parallel inputs must be 0011.

$$D_3 = 0, D_2 = 0, D_1 = 1, D_0 = 1$$

$$Ld = Q_3 Q_2$$

States 0,1,2,13,14,15 are don't-cares.

Counter Design Using S-R and J-K Flip-Flops

Procedure for Counter Design Using S-R Flip-Flops:

Instead of deriving an input equation for each D or T flip-flop, the S and R input equations must be derived.

TABLE 12-5
S-R Flip-Flop
Inputs
© Cengage Learning 2014

(a)

S	R	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

inputs not allowed

(b)

Q	Q ⁺	S	R
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0
		1	0

(c)

Q	Q ⁺	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Counter Design Using S-R and J-K Flip-Flops

TABLE 12-6

© Cengage Learning 2014

C	B	A	C^+	B^+	A^+	S_C	R_C	S_B	R_B	S_A	R_A
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	—	—	—	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	0	X	0	1	0	1
1	0	0	1	1	1	X	0	1	0	1	0
1	0	1	—	—	—	X	X	X	X	X	X
1	1	0	—	—	—	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	0	0	1


Counter Design Using S-R and J-K Flip-Flops

Counter Using S-R Flip Flops:

FIGURE 12-30

Counter of
Figure 12-22 Using
S-R Flip-Flops


© Cengage Learning 2014

 

 (a) Next-state maps

Counter Design Using S-R and J-K Flip-Flops


Counter Using S-R Flip Flops (continued):



 (b) S-R flip-flop equations

Counter Design Using S-R and J-K Flip-Flops

Counter Using S-R Flip-Flops (continued):



(c) Logic circuit

Counter Design Using S-R and J-K Flip-Flops

Procedure for Counter Design Using J-K Flip-Flops:

❖ The procedure used to design a counter with J-K flip-flops is very similar to that used for S-R flip-flops, except that J and K can be 1 simultaneously, in which case the flip-flop changes state.

TABLE 12-7
J-K Flip-Flop
Inputs

© Cengage Learning 2014

(a)			
J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b)			
Q	Q ⁺	J	K
0	0	{ 0	0
		{ 0	1
0	1	{ 1	0
		{ 1	1
1	0	{ 0	1
		{ 1	1
1	1	{ 0	0
		{ 1	0

(c)			
Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Counter Design Using S-R and J-K Flip-Flops

J-K Flip-Flop Table:

TABLE 12-8

© Cengage Learning 2014


C	B	A	C^+	B^+	A^+	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	–	–	–	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	–	–	–	X	X	X	X	X	X
1	1	0	–	–	–	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1

Counter Design Using S-R and J-K Flip-Flops


Counter Design Using J-K Flip-Flop:

FIGURE 12-31
Counter of
Figure 12-22 Using
J-K Flip-Flops

© Cengage Learning 2014

 


(a) Next-state maps

 

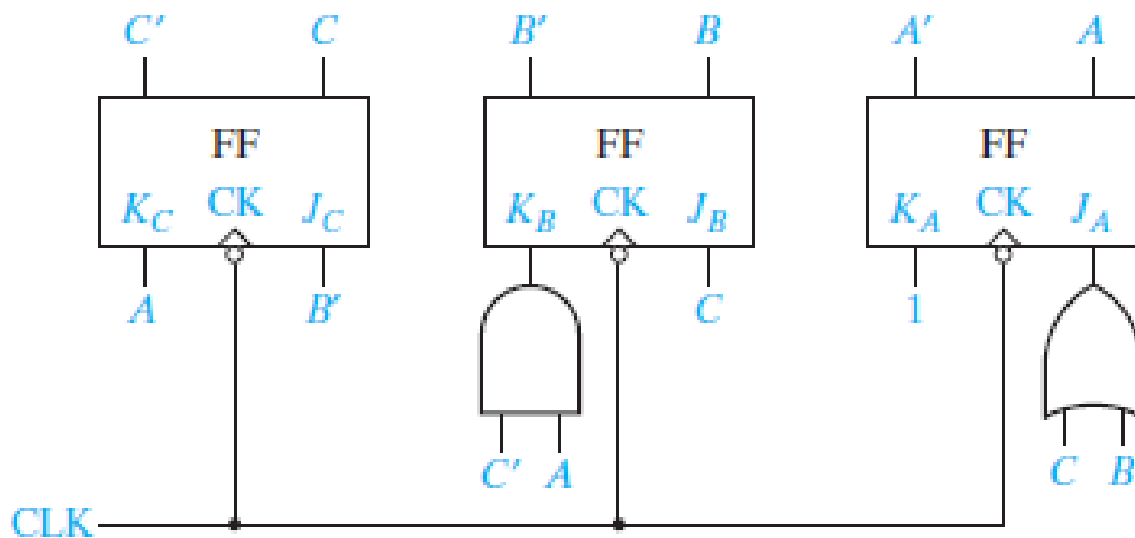(b) J-K flip-flop input equations

Counter Design Using S-R and J-K Flip-Flops

Counter Design Using J-K Flip-Flop (continued):



(c) Logic circuit (omitting the feedback lines)

Derivation of Flip-Flop Input Equations- Summary

Summary:

- ❖ The input equation for the flip-flops in a sequential circuit may be derived from the next-state equations by using truth tables or by using Karnaugh maps.
- ❖ For the D flip-flop, the input is the same as the next state.
- ❖ For the T flip-flop, the input is 1 whenever a state change is required.
- ❖ For the S-R flip-flop, S is 1 whenever the flip-flop must be set to 1 and R is 1 when it must be reset to 0.
- ❖ For a J-K flip-flop, the J and K inputs are the same as S and R, respectively, except that when one input is 1 the other input is X.

Derivation of Flip-Flop Input Equations- Summary

TABLE 12-9
Determination of
Flip-Flop Input
Equations from
Next-State
Equations
Using Karnaugh
Maps

Type of Flip-Flop	Input	$Q = 0$		$Q = 1$		Rules for Forming Input Map From Next-State Map*	
		$Q^+ = 0$	$Q^+ = 1$	$Q^+ = 0$	$Q^+ = 1$	$Q = 0$ Half of Map	$Q = 1$ Half of Map
Delay	D	0	1	0	1	no change	no change
Toggle	T	0	1	1	0	no change	complement
Set-Reset	S	0	1	0	X	no change	replace 1's with X's**
	R	X	0	1	0	replace 0's with X's**	complement
J-K	J	0	1	X	X	no change	fill in with X's
	K	X	X	1	0	fill in with X's	complement

Q^+ means the next state of Q

X is a don't-care

*Always copy X's from the next-state map onto the input maps first.

**Fill in the remaining squares with 0's.

© Cengage Learning 2014

Derivation of Flip-Flop Input Equations- Summary

Example 1:

Example
(illustrating
the use of
Table 12-9)

AB	Q	
	0	1
00	0	1
01	1	0
11	0	0
10	1	X

Q^+

Next-state map

AB	Q	
	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$D = Q'A'B + QB' + AB'$

D input map


AB	Q	
	0	1
00	0	0
01	1	1
11	0	1
10	1	X

$T = A'B + AB' + QB$

T input map

Derivation of Flip-Flop Input Equations- Summary

Example 1 (continued):

 

For the S-R flip-flop, note that when $Q = 0$, $R = X$ if $Q^+ = 0$; and when $Q = 1$, $R = 1$ if $Q^+ = 0$. Therefore, to form the R map from the Q^+ map, replace 0's with X's on the $Q = 0$ half of the map and replace 0's with 1's on the $Q = 1$ half (and fill in 0's for the remaining entries). Similarly, to form the S map from the Q^+ map, copy the 1's on the $Q = 0$ half of the map, and replace the 1's with X's on the $Q = 1$ half.