

UNIT 11

Latches and Flip-Flops

This chapter includes:

- 11.1 Introduction
- 11.2 Set- Release Latch
- 11.3 Gated Latches
- 11.4 Edge-Triggered D Flip-Flop
- 11.5 S-R Flip-Flop
- 11.6 J-K Flip-Flop
- 11.7 T Flip-Flop
- 11.8 Flip-Flops with Additional Inputs
- 11.9 Asynchronous Sequential Circuits
- 11.10 Summary

Learning Objectives

1. Explain in words the operation of S-R and gated D latches.
2. Explain in words the operation of D, D-CE, S-R, J-K, and T flip-flops.
3. Make a table and derive the characteristic (next-state) equation for such latches and flip-flops. State any necessary restrictions on the input signals.
4. Draw a timing diagram relating the input and output of such latches and flip-flops.
5. Show how latches and flip-flops can be constructed using gates. Analyze the operation of a flip-flop that is constructed of gates and latches.

Introduction

- ❖ **Sequential switching circuits** have the property that the output depends not only on the present input but also on the past sequence of inputs.
- ❖ In effect, these circuits must be able to “remember” something about the past history of the inputs in order to produce the present output.
- ❖ **Latches** and **flip-flops** are commonly used memory devices in sequential circuits.
- ❖ Basically, latches and flip-flops are memory devices which can assume one of two stable output states and which have one or more inputs that can cause the output state to change.

Introduction

Flip-Flops and Latches:

- ❖ In synchronous digital systems, it is common practice to synchronize the operation of all flip-flops by a common clock or pulse generator.
- ❖ Each of the flip-flops has a clock input, and the flip-flops are memory devices that can only change output in response to a clock input, not data inputs.
- ❖ A memory element that has no clock input is often called a latch, and we will follow this practice.

Introduction

Feedback:

- ❖ By feedback we mean that the output of one of the gates is connected back into the input of another gate in the circuit so as to form a closed loop.

FIGURE 11-1
© Cengage Learning 2014


 


FIGURE 11-2
© Cengage Learning 2014

 

Set-Release Latch

S-R Latch Explanation:

- ❖ We can construct a simple latch by introducing feedback into a NOR-gate circuit, as seen in Figure 11-3(a).
- ❖ As indicated, if the inputs are $S=R=0$, the circuit can assume a stable state with $Q=0$ and $P=1$.
- ❖ Now if we change S to 1, P will become 0. This is an unstable condition or state of the circuit because both the inputs and output of the second gate are 0; therefore Q will change to 1, leading to the stable state shown in Figure 11-3(b).

Set-Release Latch


S-R Latch Explanation (continued):

- ❖ If S is changed back to 0, the circuit will not change state because $Q=1$ feeds back into the first gate, causing P to remain 0, as shown in Figure 11-4(a).
- ❖ Note that the inputs are again $S=R=0$, but the outputs are different than those with which we started. Thus, the circuit has two different stable states for a given set of inputs.
- ❖ If we now change R to 1, Q will become 0 and P will then change back to 1, as seen in Figure 11-4(b). If we then change R back to 0, the circuit remains in this state and we are back where we started.


Set-Release Latch

FIGURE 11-3

© Cengage Learning 2014

 **FIGURE 11-4**

© Cengage Learning 2014

 

Set-Release Latch

Cross-Coupled Form of S-R Latch and S-R Latch Timing Diagram:

FIGURE 11-5
S-R Latch

© Cengage Learning 2014


 


FIGURE 11-7
Timing Diagram
for S-R Latch

© Cengage Learning 2014

 

Set-Release Latch

Present and Next States:

- ❖ The term **present state** ($Q(t)$) is used to denote the state of the Q output of the latch or flip-flop at the time any input signal changes.
- ❖ The term **next state** ($Q(t+\epsilon)$) to denote the state of the Q output after the latch or flip-flop has reacted to the input change and stabilized.

TABLE 11-1
S-R Latch Next State and Output

© Cengage Learning 2014


Present State Q	Next State Q^+				Present Output P			
	SR 00	SR 01	SR 11	SR 10	SR 00	SR 01	SR 11	SR 10
0	0	0	0	1	1	1	0	0
1	1	0	0	1	0	0	0	0

Set-Release Latch

Switch Debouncing:

A useful application of the S-R Latch involves **switch debouncing**- switch contacts tend to vibrate or bounce open and closed several times before settling down to their final position, producing a noisy transition, and this noise can interfere with the proper operation of a logic circuit.

FIGURE 11-9
Switch Debouncing
with an S-R Latch
© Cengage Learning 2014


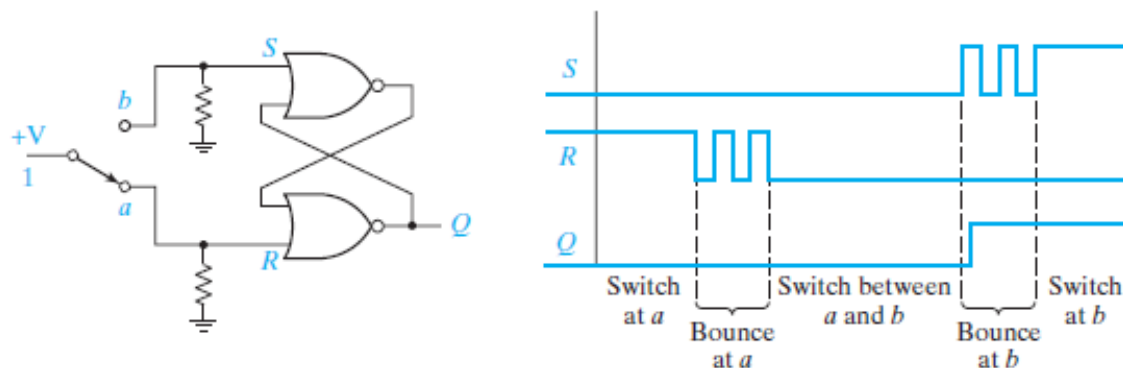


Set-Release Latch

S-R Latch using NAND Gates:

FIGURE 11-10
 \bar{S} - \bar{R} Latch

© Cengage Learning 2014

  

\bar{S}	\bar{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	} Inputs not allowed
0	0	1	

(c)

Gated Latches


Gated Latches:

- ❖ Gated latches have an additional input called the gate or enable input.
- ❖ When the gate input is inactive, which may be the high or low value, the state of the latch cannot change.
- ❖ When the gate input is active, the latch is controlled by the other inputs and operates as indicated in the preceding section.

Gated Latches

Gated S-R Latch:

FIGURE 11-11
NAND-Gate Gated
S-R Latch
© Cengage Learning 2014

 

The next-state equation is

$$Q^+ = SG + Q(R' + G')$$

and the equation for the P output is

$$P = Q' + RG$$

Gated Latches

Gated S-R Latch:

TABLE 11-2
Next-State and
Output of Gated
S-R Latch

© Cengage Learning 2014

Present State Q	Next State Q^+							
	$G = 0$				$G = 1$			
	SR 00	SR 01	SR 11	SR 10	SR 00	SR 01	SR 11	SR 10
0	0	0	0	0	0	0	1	1
1	1	1	1	1	1	0	1	1

Present State Q	Present Output P							
	$G = 0$				$G = 1$			
	SR 00	SR 01	SR 11	SR 10	SR 00	SR 01	SR 11	SR 10
0	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	0

Gated Latches

Gated D- Latch:

This latch is also referred to as a **transparent latch** since Q becomes equal to D while G is active.

FIGURE 11-14
Gated D Latch

© Cengage Learning 2014

 
 


FIGURE 11-15
Symbol and Truth
Table for Gated
Latch

© Cengage Learning 2014

D	Q	G	D	Q	Q^+
0	0	0	0	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	1	1	1

GD		00	01	11	10
Q	0	0	0	1	0
	1	1	1	1	0

$Q^+ = G'Q + GD$

Gated Latches

Edge-Triggered and Master-Slave Flip-Flops:

- ❖ If the inputs to the flip-flop only need to be stable for a short period of time around the clock edge, then we refer to the flip-flop as **edge-triggered**.
- ❖ The term **master-slave** flip-flop refers to a particular implementation that uses two gated latches in such a way that the flip-flop outputs only change on a clock edge.

Edge-Triggered D Flip-Flop

- ❖ A D flip-flop (Figure 11-17) has two inputs, D (data) and Ck (clock). The small arrowhead on the flip-flop symbol identifies the clock input.
- ❖ If the output can change in response to a 0 to 1 transition on the clock input, we say that the flip-flop is triggered on the **rising edge** (or positive edge) of the clock.
- ❖ If the output can change in response to a 1 to 0 transition on the clock input, we say that the flip-flop is triggered on the **falling edge** (or negative edge) of the clock.

Edge-Triggered D Flip-Flop

FIGURE 11-17

D Flip-Flops

© Cengage Learning 2014


 


FIGURE 11-18

Timing for
D Flip-Flop
(Falling-Edge
Trigger)


© Cengage Learning 2014

 


Edge-Triggered D Flip-Flop

D Flip-Flop (Rising-Edge Trigger):

FIGURE 11-19
D Flip-Flop (Rising-
Edge Trigger)
© Cengage Learning 2014

 

 (a) Construction from two gated D latches




(b) Timing analysis


Edge-Triggered D Flip-Flop

FIGURE 11-21
Determination of
Minimum Clock
Period


© Cengage Learning 2014

 


(a) Simple flip-flop circuit

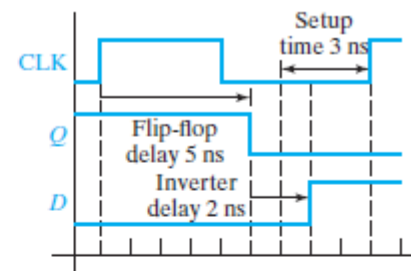

(b) Setup time not satisfied

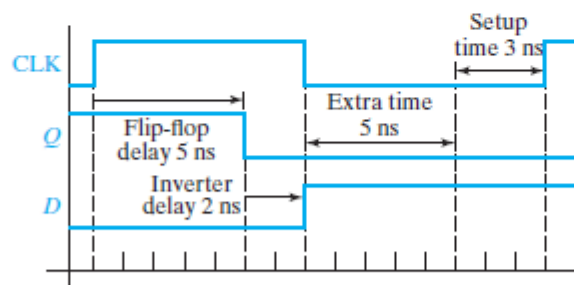

(c) Setup time satisfied

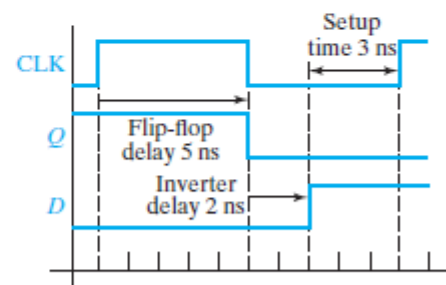


(d) Minimum clock period

S-R Flip-Flop

FIGURE 11-22
S-R Flip-Flop

© Cengage Learning 2014

 


Operation summary:


$S = R = 0$	No state change
$S = 1, R = 0$	Set Q to 1 (after active Ck edge)
$S = 0, R = 1$	Reset Q to 0 (after active Ck edge)
$S = R = 1$	Not allowed

FIGURE 11-23
S-R Flip-Flop
Implementation
and Timing

© Cengage Learning 2014

 

(a) Implementation with two latches

 

(b) Timing analysis

J-K Flip-Flop

FIGURE 11-24
J-K Flip-Flop
(Q Changes on
the Rising
Edge)

© Cengage Learning 2014




(a) J-K flip-flop

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q$$

 (b) Truth table and characteristic equation




(c) J-K flip-flop timing

J-K Flip-Flop

FIGURE 11-25
Master-Slave
J-K Flip-Flop
(Q Changes on
Rising Edge)

© Cengage Learning 2014

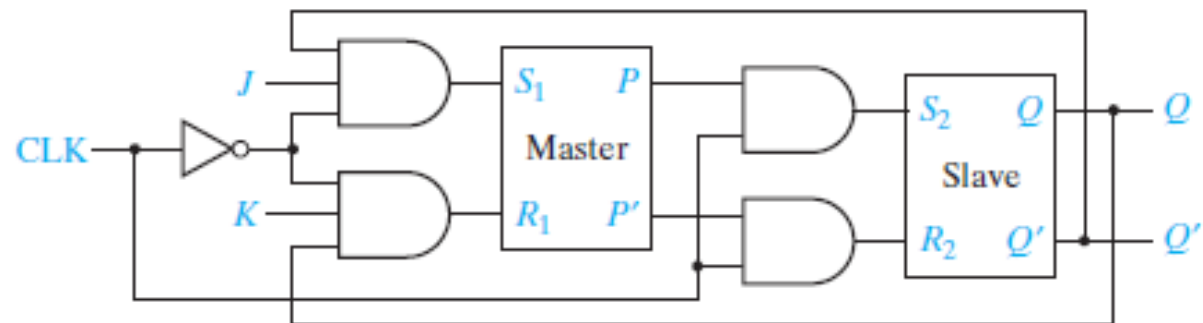


J-K Flip-Flop

FIGURE 11-26

T Flip-Flop

© Cengage Learning 2014

 

(a)

T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

(b)


$$Q^+ = T'Q + TQ' = T \oplus Q$$

T Flip-Flop

FIGURE 11-26

T Flip-Flop

© Cengage Learning 2014

 

(a)

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

(b)

$$Q^+ = T'Q + TQ' = T \oplus Q$$

Characteristic Equation
For T Flip-Flop:

$$Q^+ = JQ' + K'Q = TQ' + T'Q$$

FIGURE 11-27
Timing Diagram for
T Flip-Flop (Falling-
Edge Trigger)

© Cengage Learning 2014


 



FIGURE 11-28

Implementation
of T Flip-Flops

© Cengage Learning 2014

 

(a) Conversion of J-K to T

 


(b) Conversion of D to T

Flip-Flops with Additional Inputs

Flip-Flops with Additional Inputs:

- ❖ Flip-flops often have additional inputs which can be used to set the flip-flops to an initial state independent of the clock.

FIGURE 11-29
D Flip-Flop with
Clear and Preset
© Cengage Learning 2014

 

Ck	D	PreN	ClrN	Q^+
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)

(b)


Flip-Flops with Additional Inputs

Asynchronous Clear and Preset:

- ❖ ClrN and PreN are often referred to as **asynchronous** clear and preset inputs because their operation does not depend on the clock.

FIGURE 11-30
Timing Diagram
for D Flip-Flop
with Asynchronous
Clear and Preset

© Cengage Learning 2014

 


Flip-Flops with Additional Inputs

D Flip-Flop with Clock Enable:


FIGURE 11-31

D Flip-Flop with
Clock Enable


© Cengage Learning 2014

 

(a) Gating the clock

 

(b) D-CE symbol

 

(c) Implementation


Asynchronous Sequential Circuits

Asynchronous Sequential Circuits:

- ❖ In **asynchronous** sequential circuits the state of the circuit can change whenever any input changes.

FIGURE 11-32
Asynchronous
Circuit

© Cengage Learning 2014

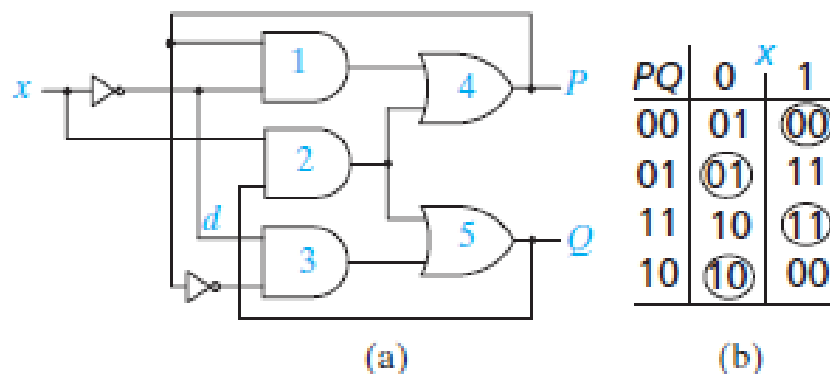

Asynchronous Sequential Circuits

Hazards and Incorrect State Transitions:

- ❖ Even if the circuit is free of hazards, delays in the “wrong” places in the circuit can cause incorrect state transitions.
- ❖ Essential hazards are properties of the next-state table; they cannot be eliminated by modifying the circuit’s logic.

Asynchronous Sequential Circuits

Multiple Input Change and Multiple-State Variable Change Examples:

FIGURE 11-33

Multiple Input
Change Example

© Cengage Learning 2014

<i>PQ</i>	00	01 ^{<i>xy</i>}	11	10
00	00	00	01	00
01	11	00	01	11
11	11	10	11	11
10	00	10	11	00

FIGURE 11-34

Multiple-State
Variable Change
Example

© Cengage Learning 2014

<i>PQR</i>	0 ^{<i>x</i>}	1
000	000	011
001	101	001
011	101	011
010	000	011
110	000	110
111	101	111
101	101	110
100	100	110

Summary

Procedure to find Characteristic Equation:

1. Make a truth table that gives the next state (Q_+) as a function of the present state (Q) and the inputs. Any illegal input combinations should be treated as don't-cares.
2. Plot a map for Q_+ and read the characteristic equation from the map.

Summary

Characteristic Equations for Various Flip-Flops/ Latches:

$$Q^+ = S + R'Q \quad (SR = 0) \quad \text{(S-R latch or flip-flop)} \quad (11-6)$$

$$Q^+ = GD + G'Q \quad \text{(gated D latch)} \quad (11-7)$$

$$Q^+ = D \cdot CE + Q \cdot CE' \quad \text{(D-CE flip-flop)} \quad (11-9)$$

$$Q^+ = JQ' + K'Q \quad \text{(J-K flip-flop)} \quad (11-10)$$

$$Q^+ = T \oplus Q = TQ' + T'Q \quad \text{(T flip-flop)} \quad (11-11)$$