



## UNIT 14

### Derivation of State Graphs and Tables

***This chapter includes:***

- 14.1 Design of a Sequence Detector
- 14.2 More Complex Design Problems
- 14.3 Guidelines for Construction of State Graphs
- 14.4 Serial Data Code Conversion
- 14.5 Alphanumeric State Graph Notation
- 14.6 Incompletely Specified State Tables

# Learning Objectives

1. Given a problem statement for the design of a Mealy or Moore sequential circuit, find the corresponding state graph and table.
2. Explain the significance of each state in your graph or table in terms of the input sequences required to reach that state.
3. Check your state graph using appropriate input sequences.


# Design of a Sequence Detector

## Sequence Detector:

- ❖ The circuit will examine a string of 0's and 1's applied to the X input and generate an output  $Z = 1$  only when a prescribed input sequence occurs.
- ❖ It will be assumed that the input X can only change between clock pulses.

**FIGURE 14-1**  
Sequence Detector  
to Be Designed

© Cengage Learning 2014

 

- ❖ The following slides use the example of a Mealy machine. See pages 460 to 463 for an example using a Moore machine.

# Design of a Sequence Detector

## State graphs:

FIGURE 14-2

© Cengage Learning 2014

 


FIGURE 14-3

© Cengage Learning 2014


 


FIGURE 14-4

Mealy State Graph  
for Sequence  
Detector

© Cengage Learning 2014

 

# Design of a Sequence Detector

## State Tables:

TABLE 14-1

© Cengage Learning 2014

Present State	Next State		Present Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_0$	$S_1$	0	0
$S_1$	$S_2$	$S_1$	0	0
$S_2$	$S_0$	$S_1$	0	1

TABLE 14-2

© Cengage Learning 2014

$AB$	$A+B+$		$Z$	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

# Design of a Sequence Detector

**Flip- Flop Next-State Maps and Map for output Z:**

		<i>X</i>	
		0	1
<i>AB</i>	00	0	0
	01	1	0
	11	X	X
	10	0	0

$$A^+ = X'B$$

		<i>X</i>	
		0	1
<i>AB</i>	00	0	1
	01	0	1
	11	X	X
	10	0	1

$$B^+ = X$$

		<i>X</i>	
		0	1
<i>AB</i>	00	0	0
	01	0	0
	11	X	X
	10	0	1

$$Z = XA$$

# Design of a Sequence Detector

## Different Types of Sequence Detectors:

**FIGURE 14-7** Different Types of Sequence Detector

Different 101 Sequence Detectors	X	0	1	0	1	0	1	1	1	0	1	0	1	0	1	1
Sliding windows, overlapping	Z	0	0	0	1	0	1	0	1	0	0	0	1	0	1	0
Sliding windows, nonoverlapping	Z	0	0	0	1	0	0	0	1	0	0	0	1	0	0	0
Sliding windows, overlapping, initial 1	Z	0	1	0	1	0	1	0	1	0	0	0	1	0	1	0
Sliding windows, nonoverlapping, initial 1	Z	0	1	0	0	0	1	0	0	0	0	0	1	0	0	0
Disjoint windows	Z	0	0	0	0	0	1	0	0	0	0	0	1	0	0	0

© Cengage Learning 2014



# More Complex Design Problems

**Desired output sequence Z for input sequence X:**


$$\begin{array}{cccccccccccccccc}
 X & = & 0 & 0 & 1 & 0 & 1 & 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 & 1 & 0 \\
 & & & & \uparrow & & \uparrow & & \uparrow & \uparrow & & & & \uparrow & & \uparrow & & & \\
 & & & & a & & b & & c & d & & & & e & & f & & & \\
 Z & = & 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 & 0
 \end{array}$$

# More Complex Design Problems

## State Graph:

FIGURE 14-8

© Cengage Learning 2014

 


State	Sequence Received
$S_0$	Reset
$S_1$	0
$S_2$	01
$S_3$	010

# More Complex Design Problems

**FIGURE 14-9**

© Cengage Learning 2014

 


State	Sequence Ends in
$S_0$	Reset
$S_1$	0 (but not 10)
$S_2$	01
$S_3$	10
$S_4$	1 (but not 01)
$S_5$	100

# More Complex Design Problems

FIGURE 14-10

© Cengage Learning 2014

 

State	Sequence Ends in
$S_0$	Reset
$S_1$	0 (but not 10)
$S_2$	01
$S_3$	10
$S_4$	1 (but not 01)
$S_5$	100

# More Complex Design Problems

## Moore Sequential Circuit:

Next, we will derive the state graph for a Moore sequential circuit with one input  $X$  and one output  $Z$ . The output  $Z$  is to be 1 if the total number of 1's received is odd and at least two consecutive 0's have been received. A typical input and output sequence is


$$\begin{array}{cccccccc}
 X = & 1 & 0 & 1 & 1 & 0 & 0 & 1 & 1 \\
 & \uparrow & & \uparrow & & \uparrow & \uparrow & \uparrow \\
 & a & & b & & c & d & e \\
 Z = & (0) & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 1
 \end{array}$$

# More Complex Design Problems

## Complete Moore State Graph and Table:

FIGURE 14-13

© Cengage Learning 2014

 

State	Input Sequences
$S_0$	Reset or even 1's
$S_1$	Odd 1's
$S_2$	Even 1's and ends in 0
$S_3$	Even 1's and 00 has occurred
$S_4$	Odd 1's and 00 has occurred
$S_5$	Odd 1's and ends in 0

# Guidelines for Construction of State Graphs

## **Guidelines:**

1. First, construct some sample input and output sequences to make sure that you understand the problem statement.
2. Determine under what conditions, if any, the circuit should reset to its initial state.
3. If only one or two sequences lead to a nonzero output, a good way to start is to construct a partial state graph for those sequences.

# Guidelines for Construction of State Graphs

## **Guidelines (continued):**

4. Another way to get started is to determine what sequences or groups of sequences must be remembered by the circuit and set up states accordingly.
5. Each time you add an arrow to the state graph, determine whether it can go to one of the previously defined states or whether a new state must be added.



# Guidelines for Construction of State Graphs

## **Guidelines (continued):**

6. Check your graph to make sure there is one and only one path leaving each state for each combination of values of the input variables.

7. When your graph is complete, test it by applying the input sequences formulated in part 1 and making sure the output sequences are correct.

# Guidelines for Construction of State Graphs

## Example 1:

### Example 1

A sequential circuit has one input ( $X$ ) and one output ( $Z$ ). The circuit examines groups of four consecutive inputs and produces an output  $Z = 1$  if the input sequence 0101 or 1001 occurs. The circuit resets after every four inputs. Find the Mealy state graph.

#### *Solution*

A typical sequence of inputs and outputs is

$$\begin{array}{cccc|cccc|cccc|cccc} X & = & 0 & 1 & 0 & 1 & 0 & 0 & 1 & 0 & 1 & 0 & 0 & 1 & 0 & 1 & 0 & 0 \\ Z & = & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \end{array}$$

The vertical bars indicate the points at which the circuit resets to the initial state. Note that an input sequence of either 01 or 10 followed by 01 will produce an output of  $Z = 1$ . Therefore, the circuit can go to the same state if either 01 or 10 is received. The partial state graph for the two sequences leading to a 1 output is shown in Figure 14-14.


Note that the circuit resets to  $S_0$  when the fourth input is received. Next, we add arrows and labels to the graph to take care of sequences which do not give a 1 output, as shown in Figure 14-15.

# Guidelines for Construction of State Graphs

## Example 1 (continued):

**FIGURE 14-14**  
Partial State  
Graph for  
Example 1

© Cengage Learning  
2014

 

State	Sequence Received
$S_0$	Reset
$S_1$	0
$S_2$	1
$S_3$	01 or 10
$S_4$	010 or 100


# Guidelines for Construction of State Graphs

## Example 1 (continued):

**FIGURE 14-15**

Complete  
State Graph  
for Example 1

© Cengage Learning  
2014

 

State	Sequence Received
$S_0$	Reset
$S_1$	0
$S_2$	1
$S_3$	01 or 10
$S_4$	010 or 100
$S_5$	Two inputs received, no 1 output is possible
$S_6$	Three inputs received, no 1 output is possible

❖ See pages 469-472 for more examples.



# Serial Data Code Conversion

## Serial Data Code Converter:

❖ Binary data is frequently transmitted between computers as a serial stream of bits.

**FIGURE 14-19**  
Serial Data  
Transmission

© Cengage Learning 2014

 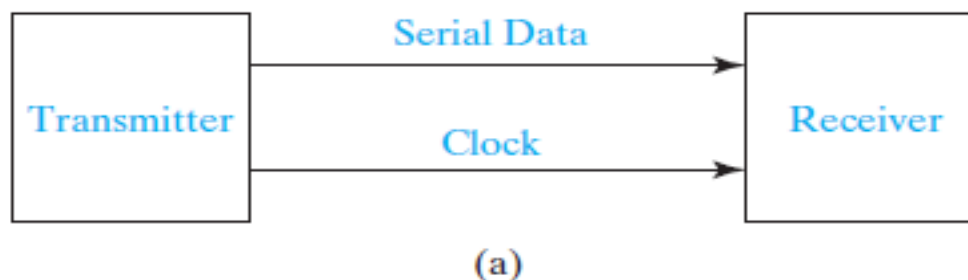


# Serial Data Code Conversion

## Coding Schemes for Serial Data Transmission:

**FIGURE 14-20**  
Coding Schemes  
for Serial Data  
Transmission

© Cengage Learning 2014

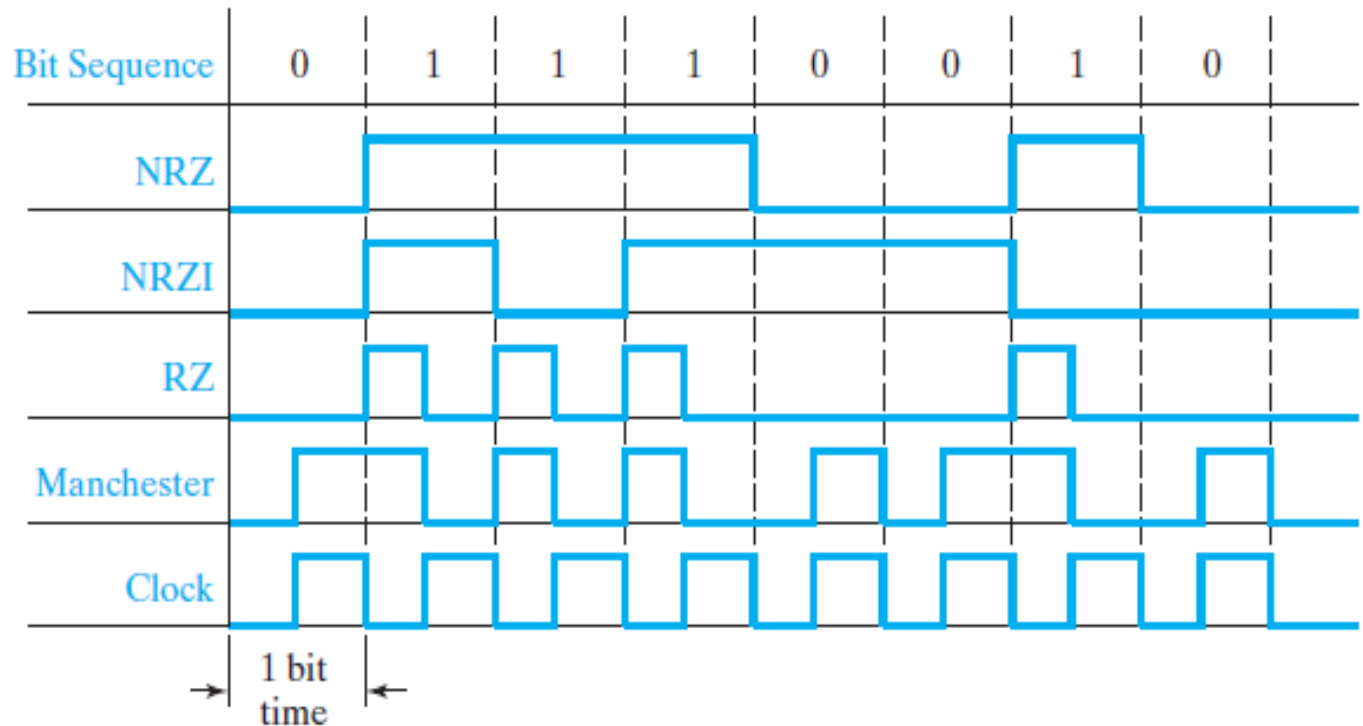


# Serial Data Code Conversion


## Mealy Circuit for NRZ to Manchester Conversion:

**FIGURE 14-21**  
Mealy Circuit for  
NRZ to Manchester  
Conversion

© Cengage Learning 2014

 


(a) Conversion circuit

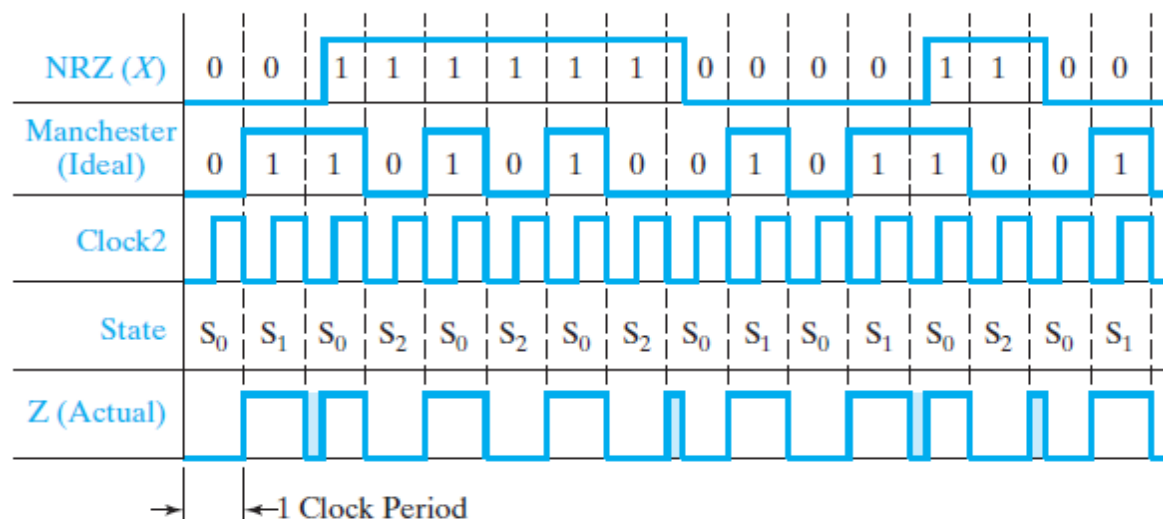

(b) Timing chart

# Serial Data Code Conversion
 
## Mealy Circuit for NRZ to Manchester Conversion (continued):



(c) State graph

Present State	Next State		Output (Z)	
	X = 0	X = 1	X = 0	X = 1
$S_0$	$S_1$	$S_2$	0	1
$S_1$	$S_0$	–	1	–
$S_2$	–	$S_0$	–	0


(d) State table



# Serial Data Code Conversion

## Moore Circuit for NRZ to Manchester Conversion:


**FIGURE 14-22**  
Moore Circuit for  
NRZ to Manchester  
Conversion  
© Cengage Learning 2014

 

(a) Timing chart

# Serial Data Code Conversion
 
## Moore Circuit for NRZ to Manchester Conversion (continued):



(b) State graph

Present State	Next State		Present Output (Z)
	X = 0	X = 1	
$S_0$	$S_1$	$S_3$	0
$S_1$	$S_2$	—	0
$S_2$	$S_1$	$S_3$	1
$S_3$	—	$S_0$	1

(c) State table


# Alphanumeric State Graph Notation

## Alphanumeric State Graph Notation:

❖ When a state sequential circuit has several inputs, it is often convenient to label the state graph arcs with alphanumeric input variable names instead of 0's and 1's.

**FIGURE 14-23**  
State Graphs with  
Variable Names on  
Arc Labels

© Cengage Learning 2014

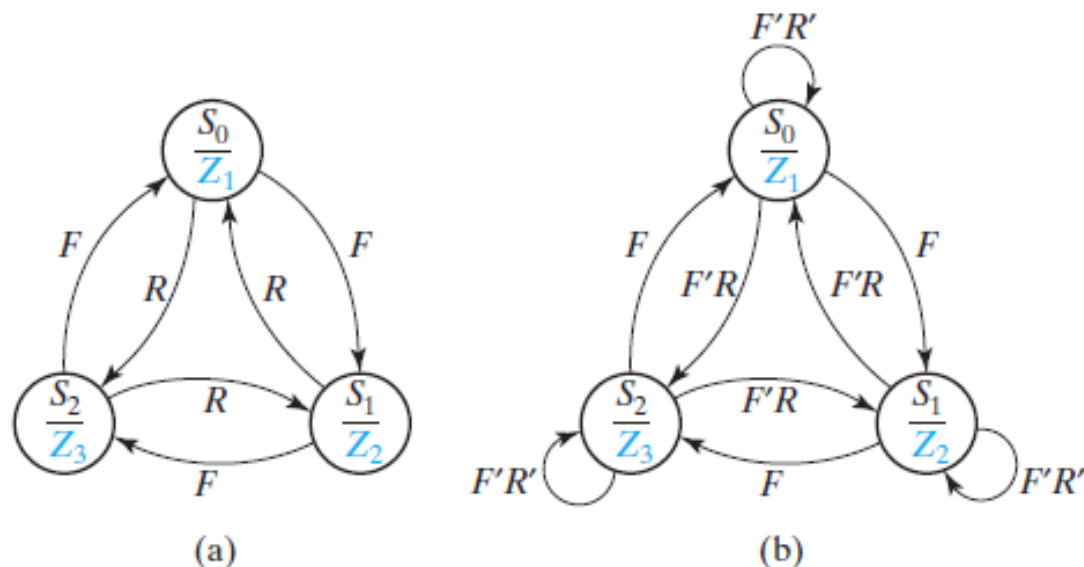

# Alphanumeric State Graph Notation

**TABLE 14-8**  
State Table for  
Figure 14-23

© Cengage Learning 2014

PS	NS				Output		
	<i>FR</i> = 00	01	10	11	<i>Z</i> <sub>1</sub>	<i>Z</i> <sub>2</sub>	<i>Z</i> <sub>3</sub>
<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>1</sub>	1	0	0
<i>S</i> <sub>1</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>2</sub>	0	1	0
<i>S</i> <sub>2</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	0	0	1

# Alphanumeric State Graph Notation

## Properties of Completely Specified State Graphs:

- (1) When we OR together all input labels on arcs emanating from a state, the result reduces to 1.
- (2) When we AND together any pair of input labels on arcs emanating from a state, the result is 0.
- ❖ Property (1) ensures that for every input combination, at least one next state is defined.
- Property (2) ensures that for every input combination, no more than one next state is defined.
- ❖ If both properties are true, then exactly one next state is defined, and the graph is properly specified.

# Alphanumeric State Graph Notation

## Mealy State Graph Notation:

We will use the following notation on Mealy state graphs for sequential circuits:  $X_i X_j / Z_p Z_q$  means if inputs  $X_i$  and  $X_j$  are 1 (we don't care what the other input values are), the outputs  $Z_p$  and  $Z_q$  are 1 (and the other outputs are 0). That is, for a circuit with four inputs ( $X_1, X_2, X_3$ , and  $X_4$ ) and four outputs ( $Z_1, Z_2, Z_3$ , and  $Z_4$ ),  $X_1 X_4' / Z_2 Z_3$  is equivalent to 1--0/0110. This type of notation is very useful for large sequential circuits where there are many inputs and outputs.


We will use a dash to indicate that all inputs are don't-cares. For example, an arc label  $-/Z_1$  means that for any combination of input values, the indicated state transition will occur and the output  $Z_1$  will be 1.

# Incompletely Specified State Tables

## BCD Parity Detector:

A Mealy model sequential circuit examines the input sequence and generates an output of 1 when the last bit of a BCD digit is received if the parity of the digit is even; otherwise, the sequential circuit output is 0.

**FIGURE 14-24**  
State Graph for  
BCD Parity Detector  
© Cengage Learning 2014

 

# Incompletely Specified State Tables

**TABLE 14-9**  
State Table for  
Figure 14-24

© Cengage Learning 2014


Present State	Next State		Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_1$	$S_2$	0	0
$S_1$	$S_3$	$S_4$	0	0
$S_2$	$S_5$	—	0	—
$S_3$	$S_6$	$S_7$	0	0
$S_4$	$S_7$	$S_6$	0	0
$S_5$	$S_7$	—	0	—
$S_6$	$S_0$	$S_0$	1	0
$S_7$	$S_0$	$S_0$	0	1



# Incompletely Specified State Tables

**FIGURE 14-25**  
Disjoint Window  
101 Detector

© Cengage Learning 2014

 

**TABLE 14-10**  
State Table for  
Figure 14-25

© Cengage Learning 2014

Present State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	—	—
S <sub>1</sub>	S <sub>3</sub>	S <sub>3</sub>	—	—
S <sub>2</sub>	S <sub>4</sub>	S <sub>3</sub>	—	—
S <sub>3</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
S <sub>4</sub>	S <sub>0</sub>	S <sub>0</sub>	0	1